

9 gennaio 2004

$$1^\circ) i_T(0^+) = 1.0 \text{ A}$$

$$2^\circ) \cos \Phi = 0.84$$

16 aprile 2004

$$1^\circ) P_E = 192 \text{ W}$$

$$P_L = 48 \text{ W}$$

$$E_L = 128 \text{ mJ}$$

$$2^\circ) P_3 = 1.7 \text{ kW}$$

$$\cos \Phi_{23} = 0.53$$

$$C_\Delta = 7 \text{ }\mu\text{F}$$

25 giugno 2004

$$1^\circ) P = 288 \text{ W}$$

$$2^\circ) C_\Delta = 49.5 \text{ }\mu\text{F}$$

9 luglio 2004

$$1^\circ) i(0^+) = -1.428 \text{ A}$$

$$2^\circ) \cos \Phi = 0.244$$

10 settembre 2004

$$1^\circ) Q = 6.7 \mu\text{ C}$$

$$2^\circ) \cos \Phi = 0.997$$

$$Q = -9.8 \text{ kVAr}$$

8 ottobre 2004

$$1^\circ) p_E = 23.6 \text{ W}$$

$$Q = 11.25 \text{ }\mu\text{C}$$

$$W_m = 1.58 \text{ mJ}$$

$$2^\circ) \cos \Phi_1 = 0.242$$

$$C_Y = 1.14 \text{ mF}$$

10 Gennaio 2005

$$1^{\circ}) i = 0.6 \text{ A}$$

$$W_m = 18 \text{ mJ}$$

$$v = 4.32 \text{ V}$$

$$p_E = 51.1 \text{ W}$$

$$2^{\circ}) \cos \Phi = 0.441$$

$$Q = 13.2 \text{ kVAr}$$

$$C_{\Delta} = 197 \text{ }\mu\text{F}$$

18 marzo 2005

$$1^{\circ}) i = 2.8 \text{ A}$$

$$W_e = 0.0345 \text{ mJ}$$

$$v = -7.2 \text{ V}$$

$$p_E = 52.8 \text{ W}$$

$$2^{\circ}) \cos \Phi_{U1} = 0.447$$

$$\cos \Phi_{U2} = 0.707$$

$$\cos \Phi_{U1+U2} = 0.840$$

20 Maggio 2005

$$1^{\circ}) i = 0.077 \text{ A}$$

$$W_m = 1.7 \text{ mJ}$$

$$v = 14.15 \text{ V}$$

$$p_I = 2.346 \text{ W}$$

$$2^{\circ}) \cos \Phi = 0.335$$

$$P = 28.1 \text{ kW}$$

$$C_Y = 1.75 \text{ mF}$$

24 Giugno 2005

$$1^{\circ}) i = 43 \text{ mA}$$

$$W_e = 21.8 \text{ }\mu\text{J}$$

$$v = 12.8 \text{ V}$$

$$p_{GT} = 25.7 \text{ W}$$

$$2^{\circ}) I_{l,eff} = 9.12 \text{ A}$$

$$\alpha_{II} = 142^{\circ}$$

$$Q_{GT,e} = 336 \text{ VAr}$$

$$Q_{C,a} = -48 \text{ VAr}$$

$$P_{GC,e} = 32 \text{ W}$$

7 Ottobre 2005

$$1^{\circ}) i = 1.35 \text{ A}$$

$$W_m = 166 \text{ } \mu\text{J}$$

$$v = -3.48 \text{ V}$$

$$p_{GT} = 6.6 \text{ W}$$

$$2^{\circ}) P_{R,a} = 3.2 \text{ W}$$

$$P_{GT,e} = -54 \text{ W}$$

$$Q_{GC,e} = -91.7 \text{ Var}$$

9 Dicembre 2005

$$1^{\circ}) i = 1.236 \text{ A}$$

$$W_e = 2.44 \text{ mJ}$$

$$v = -2.21 \text{ V}$$

$$p_{GT} = 13.26 \text{ W}$$

$$2^{\circ}) I_{l,eff} = 9.12 \text{ A}$$

$$\alpha_{II} = 142^{\circ}$$

$$Q_{GT,e} = 336 \text{ VAr}$$

$$Q_{C,a} = -120 \text{ VAr}$$

$$P_{GC,e} = 75.2 \text{ W}$$

13 Gennaio 2006

$$1^{\circ}) i = 0.077 \text{ A}$$

$$W_m = 1.7 \text{ mJ}$$

$$v = 14.15 \text{ V}$$

$$p_I = 1.846 \text{ W}$$

$$2^{\circ}) \cos \Phi = 0.335$$

$$P = 9.4 \text{ kW}$$

$$C_{\Delta} = 194 \text{ } \mu\text{F}$$