

$$v(t) = V_m \cos(\omega t + \alpha_v) \quad \varphi = \alpha_v - \alpha_i$$

$$i(t) = I_m \cos(\omega t + \alpha_i)$$

POT. ASSORBITA Istantanea

$$p(t) = v(t) i(t) = V_m I_m \cos(\omega t + \alpha_v) \cos(\omega t + \alpha_i)$$

$$\begin{aligned} i(t) &= I_m \cos(\omega t + \alpha_i + \alpha_v - \alpha_v) = I_m \cos(\omega t + \alpha_v - \varphi) = \\ &= I_m \cos \varphi \cos(\omega t + \alpha_v) + I_m \sin \varphi \sin(\omega t + \alpha_v) = i_1(t) + i_2(t) \end{aligned}$$

$$i_1(t) = I_m \cos \varphi \cos(\omega t + \alpha_v) \quad \text{CORRENTE Istantanea ATTIVA}$$

$$i_2(t) = I_m \sin \varphi \sin(\omega t + \alpha_v) \quad \text{" " REATTIVA}$$

$$p(t) = v(t) [i_1(t) + i_2(t)] = v(t) i_1(t) + v(t) i_2(t)$$

$$p_1(t) = v(t) i_1(t) = V_m I_m \cos \varphi \cos^2(\omega t + \alpha_v) \quad \text{POT. Istant. ATTIVA}$$


$$p_2(t) = v(t) i_2(t) = V_m I_m \sin \varphi \frac{1}{2} \sin(2\omega t + 2\alpha_v) \quad \text{POT. Istant. REATTIVA}$$

$$P_e(t) = V_{\text{eff}} I_{\text{eff}} \cos \varphi \cos^2(\omega t + \alpha_v) \quad \cos \varphi > 0 \Rightarrow P_e(t) \geq 0$$

$$\cos \varphi < 0 \Rightarrow P_e(t) \leq 0$$

FLUSSO DI POTENZA UNIDIREZIONALE
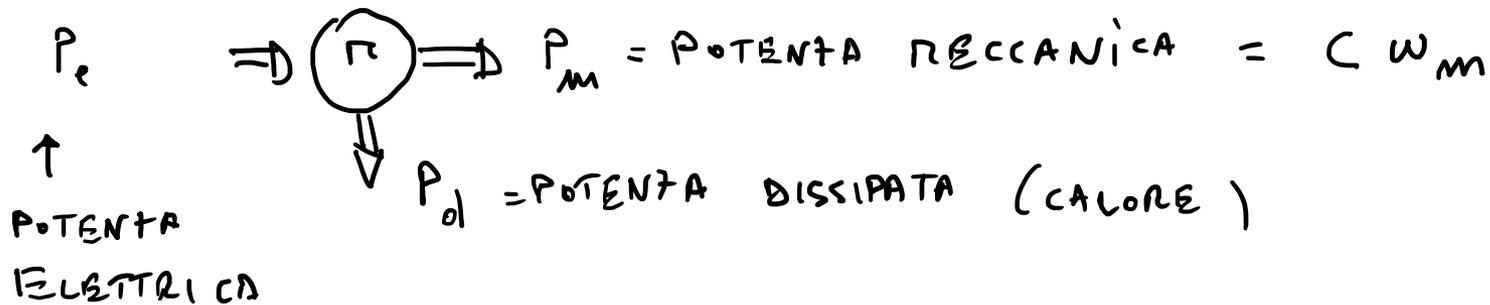
$$P_2(t) = \frac{V_{\text{eff}} I_{\text{eff}}}{2} \sin \varphi \sin(2\omega t + 2\alpha_v) \quad \text{FLUSSO DI POTENZA OSCILLANTE}$$



$$\eta = \text{RENDIMENTO} = \frac{P_m}{P_e} = \frac{\Delta E_m}{\Delta E_e} \approx \frac{\langle P_m \rangle (t_2 - t_1)}{\langle P_e \rangle (t_2 - t_1)}$$

$$\Delta E_m = \int_{t_1}^{t_2} P_m(t) dt \quad \text{ENERGIA MECCANICA EROGATA} \quad t_2 - t_1 \gg T = \frac{1}{f}$$

$$\Delta E_e = \int_{t_1}^{t_2} P_e(t) dt \quad \text{ENERGIA ELETTRICA ASSORBITA}$$

$$P = \text{POTENZA ATTIVA} = \frac{1}{T} \int_0^T p(t) dt \quad (\text{W})$$

$$P = \frac{1}{T} \int_0^T [p_e(t) + p_r(t)] dt = \frac{1}{T} \int_0^T p_e(t) dt + \frac{1}{T} \int_0^T p_r(t) dt =$$

$$= \frac{1}{T} \int_0^T V_m I_m \cos \varphi \cos^2(\omega t + \alpha_v) dt + \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \sin \varphi \sin(2\omega t + 2\alpha_v) dt$$

$$\quad \quad \quad \parallel \quad \quad \quad \parallel$$


$$\quad \quad \quad \frac{V_m I_m}{2} \cos \varphi \quad \quad \quad 0$$

$$P = \frac{V_m I_m}{2} \cos \varphi = V_e I_e \cos \varphi$$

$\cos \varphi = \text{FATTORE DI POTENZA}$

$$V_e = \frac{V_m}{\sqrt{2}}, \quad I_e = \frac{I_m}{\sqrt{2}}$$
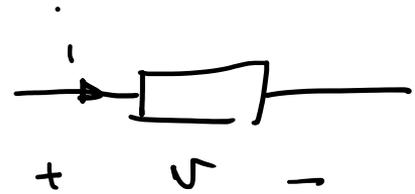
$$N = \text{POTENZA COMPLESSA} = \underline{V} \underline{I}^*$$



$$\underline{I}^* = \text{COMPLESSO CONIUGATO DI } \underline{I}$$

$$\varphi = \alpha_v - \alpha_i$$

ESERPIO $\underline{I} = 3 + j2$ $\underline{I}^* = 3 - j2$

$$\underline{V} = V_e e^{j\alpha_v}$$

$$\underline{I} = I_e e^{j\alpha_i}$$

$$\underline{I}^* = I_e e^{-j\alpha_i}$$

$$N = V_e e^{j\alpha_v} I_e e^{-j\alpha_i} = V_e I_e e^{j\varphi} = \underbrace{V_e I_e \cos \varphi}_P + j \underbrace{V_e I_e \sin \varphi}_Q$$

$$Q = \text{POT. REATTIVA} = V_e I_e \sin \varphi \quad (\text{VAR})$$

VOLT-AMPERE-REATTIVO

BILANCIO ENERGETICO DI UN CIRCUITO IN CORRENTE


ALTERNATA

$$\sum_{k=1}^R N_k = 0$$

$$\sum_{k=1}^R (P_k + iQ_k) = 0$$

$$\left\{ \begin{array}{l} \sum_{k=1}^R P_k = 0 \\ \sum_{k=1}^R Q_k = 0 \end{array} \right.$$

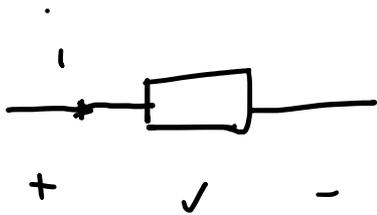È NULLA LA SOMMA DELLE POTENZE COMPLESSE ASSORBITE DA TUTTI I COMPONENTI



$$P = \frac{1}{T} \int_0^T p(t) dt = V_e I_e \cos \varphi \quad (\text{W})$$

$$N = \underline{V} \underline{I}^* = V_e I_e \cos \varphi + j V_e I_e \sin \varphi = P + iQ$$

$$Q = V_e I_e \sin \varphi \quad (\text{VAR})$$

$$A = \text{POT. APPARENTE} = |N| = |\underline{V} \underline{I}^*| = |\underline{V}| |\underline{I}^*| = V_e I_e = \sqrt{P^2 + Q^2}$$

(VA) (VOLT-AMPERE)

$$\underline{V} = V_e e^{i\alpha_v}$$



$$\begin{aligned} |\underline{V}| &= V_e |e^{i\alpha_v}| = V_e |\cos\alpha_v + i\sin\alpha_v| = \\ &= V_e \sqrt{\cos^2\alpha_v + \sin^2\alpha_v} = V_e \end{aligned}$$


$$\underline{I} = I_e e^{i\alpha_i}$$

$$|\underline{I}| = I_e$$

$$\underline{I}^* = I_e e^{-i\alpha_i}$$

$$|\underline{I}^*| = I_e$$

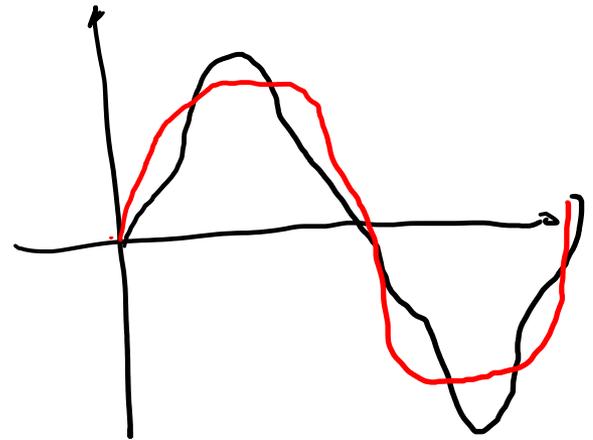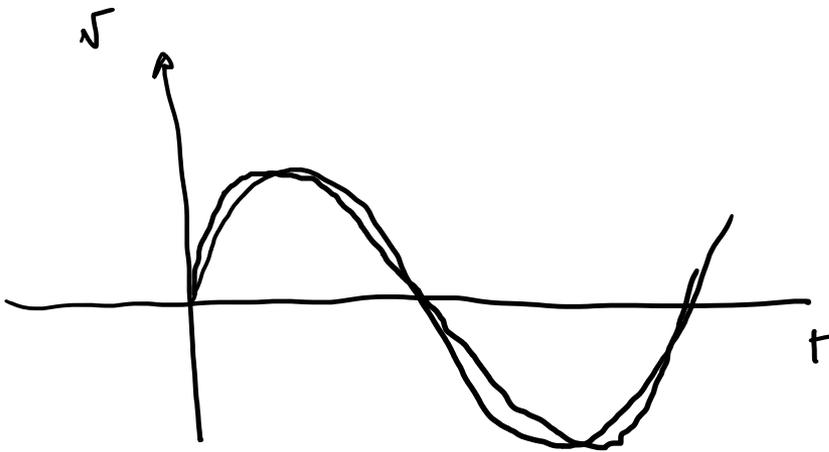

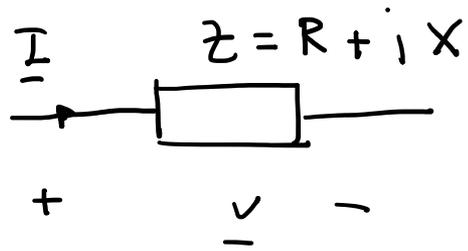

$$\underline{V} = z \underline{I} = (R + jX) \underline{I}$$

$$N = \underline{V} \underline{I}^* = \left[(R + jX) \underline{I} \right] \underline{I}^* = (R + jX) \left[\underline{I} \underline{I}^* \right]$$

$$c = a + jb$$

$$c^* = a - jb$$

$$c c^* = (a + jb)(a - jb) = a^2 + b^2 = |c|^2$$

$$N = (R + jX) |\underline{I}|^2 = (R + jX) \underline{I}_e^2 = R \underline{I}_e^2 + jX \underline{I}_e^2 = P + jQ$$

$$P = R \underline{I}_e^2 \quad \text{Pot. ATTIVA}$$

$$Q = X \underline{I}_e^2 \quad \text{Pot. REATTIVA}$$



$$Z = R$$

$$P = R I_e^2 > 0$$


$$Q = 0 \quad I_e^2 = 0$$



$$Z = j\omega L$$

$$P = 0 \quad I_e^2 = 0$$


$$Q = \omega L I_e^2 > 0$$

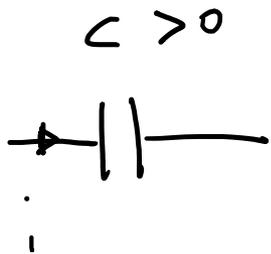

$$Z = -\frac{j}{\omega C}$$

$$P = 0 \quad I_e^2 = 0$$

$$Q = -\frac{1}{\omega C} I_e^2 < 0$$

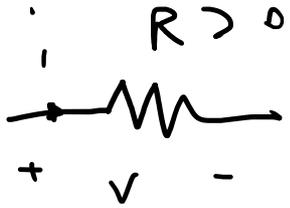




$$\underline{V} = R \underline{I}$$

$$\underline{V} = R I_e e^{j\alpha_i}$$

V_e

$$V_e = R I_e$$
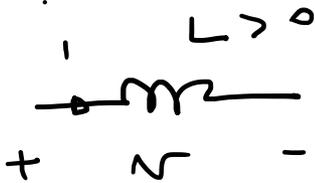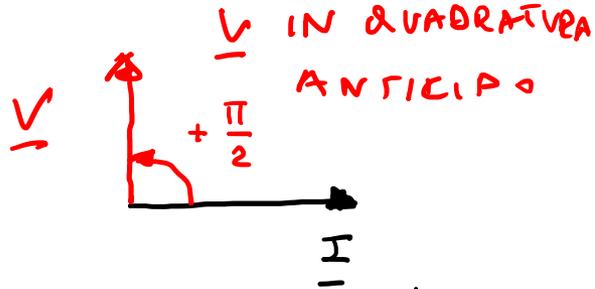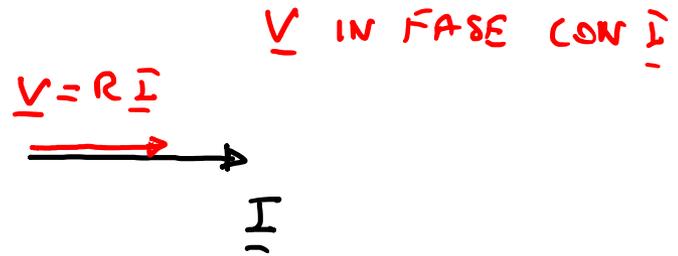
$$\alpha_v = \alpha_i \quad \varphi = 0$$



$$\underline{V} = j\omega L \underline{I}$$



$$= j\omega L I_e e^{j\alpha_i} = e^{j\frac{\pi}{2}} \omega L I_e e^{j\alpha_i} = \omega L I_e e^{j(\alpha_i + \frac{\pi}{2})}$$

V_e α_v

$$V_e = \omega L I_e$$

$$\alpha_v = \alpha_i + \frac{\pi}{2} \quad \varphi = \frac{\pi}{2}$$

V IN QUADRATURA RITARDATA

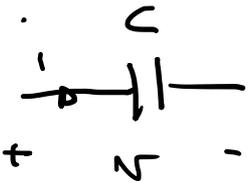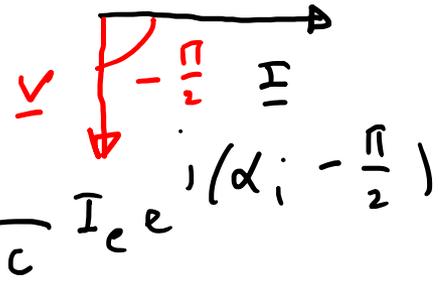



$$\underline{V} = -\frac{1}{\omega C} \underline{I}$$

$$= \frac{1}{\omega C} I_e e^{j\alpha_i} e^{-j\frac{\pi}{2}} = \frac{1}{\omega C} I_e e^{j(\alpha_i - \frac{\pi}{2})}$$

$$V_e = \frac{I_e}{\omega C}$$
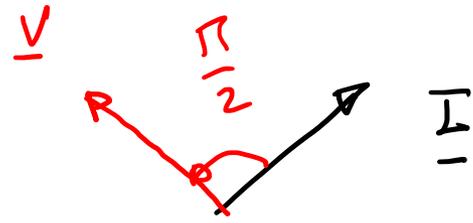
$$\alpha_v = \alpha_i - \frac{\pi}{2} \quad \varphi = -\frac{\pi}{2}$$



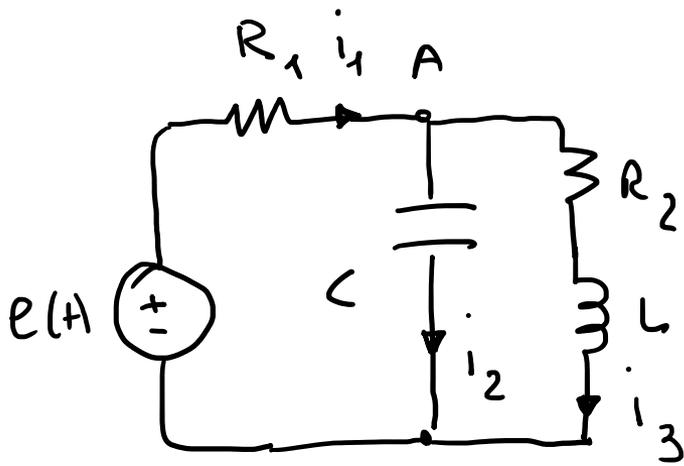

B

$$\omega = 2\pi f = 2 \times \pi \times 50 =$$

$$= 314.2 \frac{\text{rad}}{\text{s}}$$

$$t' = t - \Delta t \Rightarrow t = t' + \Delta t$$

$$e(t') = E_n \cos(\omega t' + \omega \Delta t + \alpha) = E_n \cos(\omega t' + \alpha')$$

$$i_1(t') = I_{1n} \cos(\omega t' + \omega \Delta t + \alpha_1) = I_{1n} \cos(\omega t' + \alpha_1')$$

$$R_1 = 2 \Omega, R_2 = 3 \Omega, C = 0.2 \text{ mF}$$

$$L = 4 \text{ mH}$$

$$e(t) = E_n \cos(\omega t + \alpha) \quad \underline{\underline{\alpha = 0}}$$

$$E_n = 10 \text{ V} \quad f = 50 \text{ Hz}$$

$$i_1(t) = I_{1n} \cos(\omega t + \alpha_1)$$

$$i_2(t) = I_{2n} \cos(\omega t + \alpha_2)$$

$$i_3(t) = I_{3n} \cos(\omega t + \alpha_3)$$

$$\alpha' = \alpha + \omega \Delta t \quad \alpha' - \alpha_1' = \alpha - \alpha_1$$

$$\alpha_1' = \alpha_1 + \omega \Delta t$$

UNA QUALSIASI GRANDEZZA PUO' ESSERE PRESA COME GRANDEZZA DI RIFERIMENTO PER GLI ANGOLI DI FASE (FASE = 0)