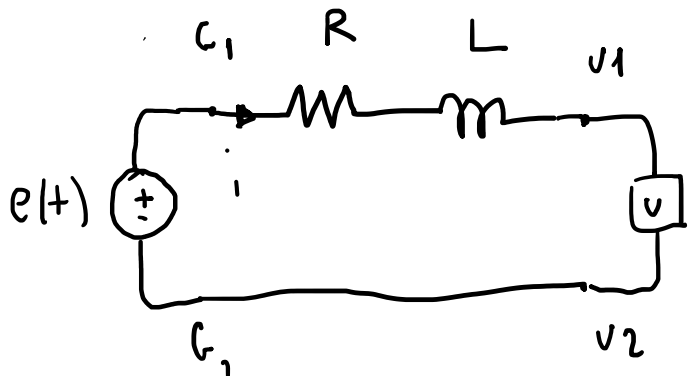


$$R_{CAVO} = \rho \frac{L}{S}$$

$$R = 2 R_{CAVO}$$


LINEA CORTA




$$\nabla \times \vec{E} = - \frac{\partial \vec{B}}{\partial t} \neq 0$$

$$\int_A^B \vec{E} \cdot d\vec{e} = \int_A^B \vec{E} \cdot d\vec{e} = V_{AB}$$
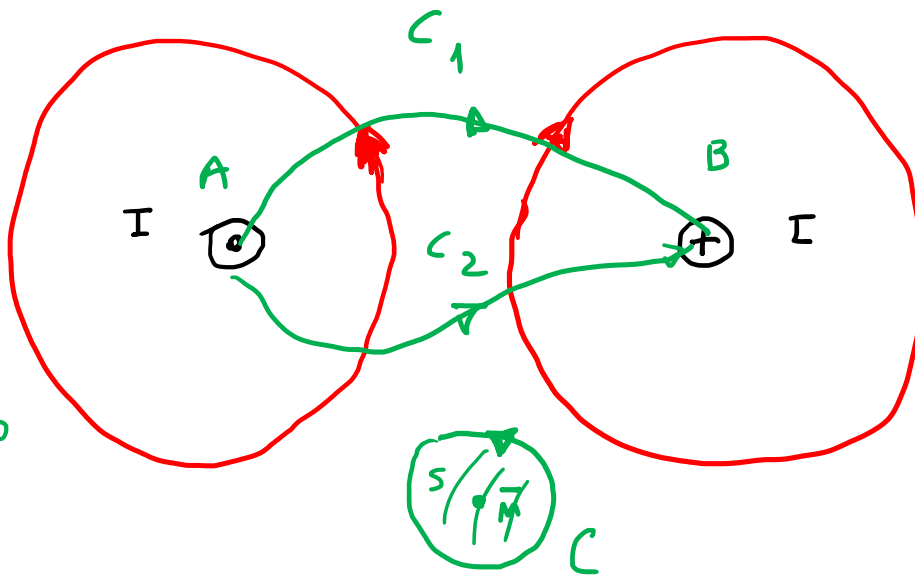
$$\oint_C \vec{E} \cdot d\vec{e} = - \frac{\partial q}{\partial t} \quad \int_S \vec{B} \cdot \vec{n} ds = 0$$



$$z = z_0$$

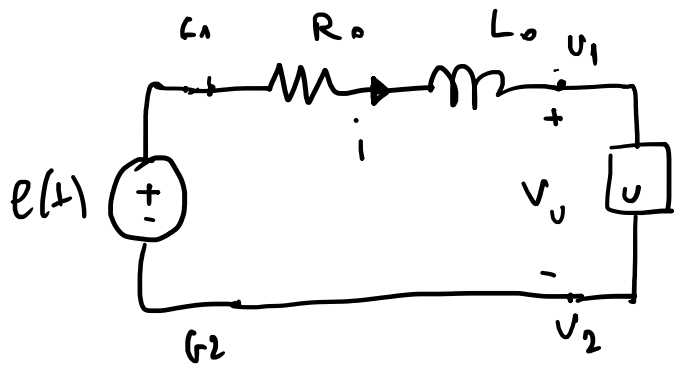

$$f = 50 \text{ Hz} \quad , \quad V_{v,e} = 210 \text{ V}$$

$$P_v = 8 \text{ kW} \quad , \quad \cos \varphi_v = 0.6 \quad , \quad \varphi_v > 0$$

$$R_0 = 0.2 \Omega \quad , \quad \omega L_0 = 0.3 \Omega$$

$$-\underline{E} + (R_0 + j\omega L_0) \underline{I} + \underline{V}_v = 0$$

$$\underline{V}_v = V_{ve} e^{j\varphi_v} = 210 [\cos \varphi_v + j \sin \varphi_v]$$

$$\varphi_v = \cos^{-1}(0.6) = 0.9273 \text{ rad}$$

$$\underline{V}_v = 126 + j168$$

$$P_v = V_{ve} I_e \cos \varphi_v = 8 \text{ kW} \Rightarrow I_e = \frac{P_v}{V_{ve} \cos \varphi_v} =$$

$$I_e = \frac{8 \times 10^3}{210 \times 0.6} = 63.49 \text{ A}$$

$$\underline{I} = 63.49$$

$$\underline{E} = \underline{V}_v + (R_0 + j\omega L_0) \underline{I} = 126 + j168 + (0.2 + j0.3) \times 63.49 = 138.7 + j187$$

$$E_e = \sqrt{138.7^2 + 187^2} = 232.8 \text{ V}$$


$$\underline{I} = I_e \quad \text{RIFERIMENTO}$$

ANGOLI DI FASE

$$\alpha_i = 0$$

$$\varphi_v = \alpha_{v_v} - \alpha_i$$

$$\alpha_{v_v} = \varphi_v$$

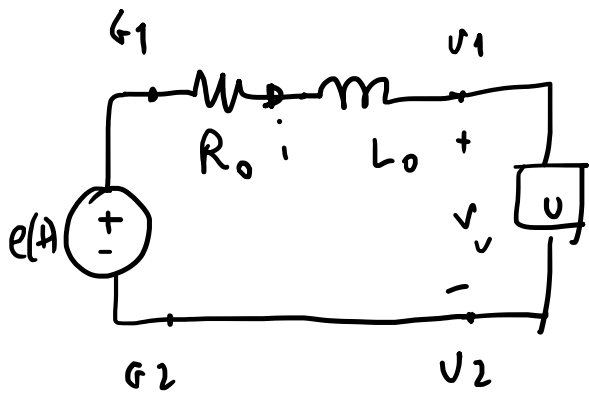

$$I_e = \frac{P_v}{V_{v,e} \cos \varphi_v} = 63.49 \text{ A}$$

$$P_o = R_o I_e^2 = 0.2 \times 63.49^2 = 806.2 \text{ W}$$

$$Q_o = \omega L_o I_e^2 = 0.3 \times 63.49^2 = 1209 \text{ VAR}$$


$$P_v = 8000 \text{ W}$$

$$Q_v = P_v \tan \varphi_v = 8000 \times \tan(0.8273) = 8000 \times 1.333 = 10667 \text{ VAR}$$

$$P_E = P_o + P_v = 806.2 + 8000 = 8806.2 \text{ W}$$

$$Q_E = Q_o + Q_v = 1209 + 10667 = 11876 \text{ VAR}$$
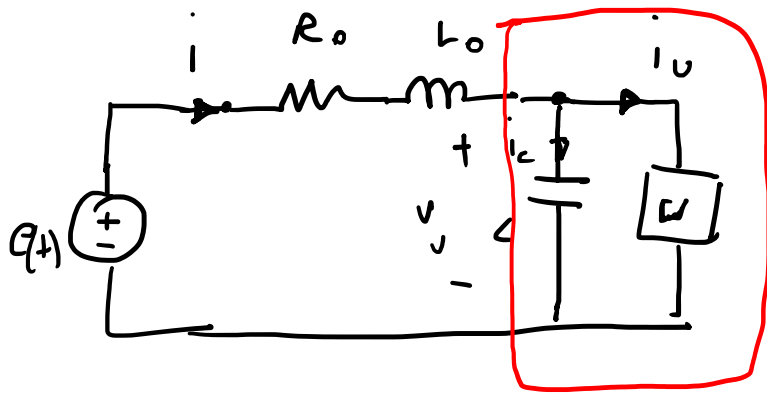
$$A_E = E_e I_e = \sqrt{P_E^2 + Q_E^2} \Rightarrow E_e = \frac{\sqrt{8806^2 + 11876^2}}{63.49} = 232.9 \text{ V}$$



$$V_{v,e} = 210 \text{ V}, \quad P_V = 8000 \text{ W}$$

$$\cos \varphi_v = 0.6, \quad \varphi_v > 0$$

$$\cos \varphi = 0.9, \quad \varphi > 0, \quad f = 50 \text{ Hz}$$

$$\varphi = \cos^{-1}(0.9) = 0.451 \text{ rad}$$

$$C = \frac{P_V \cdot (\tan \varphi_v - \tan \varphi)}{\omega V_{v,e}^2} = \frac{8000 (\tan(0.9273) - \tan(0.451))}{2 \times \pi \times 50 \times 210^2} =$$

$$= 4.9 \times 10^{-4} \text{ F}$$

$$I_e = \frac{P_V}{V_{v,e} \cos \varphi} = \frac{8000}{210 \times 0.9} = 42.33 \text{ A}$$

$$P_o = R_o I_e^2 = 0.2 \times 42.33^2 = 358.4 \text{ W}$$

$$Q_o = \omega L_o I_e^2 = 0.3 \times 42.33^2 = 537.5 \text{ VAR}$$

$$P_E = P_o + P_V = 8000 + 358.4 = 8358 \text{ W}$$

$$Q'_V = P'_V \cdot \tan \varphi =$$

$$= 8000 \times \tan(0.451) =$$

$$= 3874 \text{ VAR}$$

$$Q_E = Q_o + (Q_V + Q_C) = Q_o + Q'_V = 537.5 + 3874 = 4411 \text{ VAR}$$

$$E_c = \frac{\sqrt{P_E^2 + Q_E^2}}{I_e} = 223.3 \text{ V}$$

$$I_e = \frac{P}{V_e \cos \varphi}$$

$$P_0 = R_0 I_e^2$$

$$R_0 = \rho \frac{L}{S_{\text{CAVO}}}$$

GENERATORE SINCRONO TRIFASE

STATORE


$P = \text{NUMERO DI COPPIE DI POLI}$

$$\omega = p \omega_m$$


ROTORE

CAMPO ROTANTE

$$\omega_c = \omega_m$$

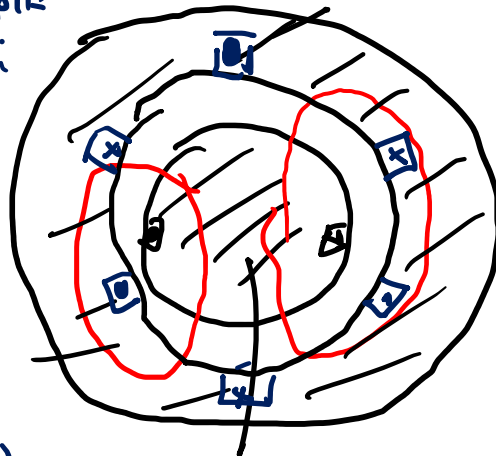

ROTORE

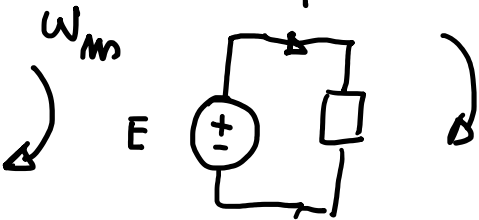


$i = \text{COSTANTE NEL TEMPO (C.C.)}$

$$e_{10}(t) = E_{0\pi} \cos(\omega t + \alpha_1)$$

$$e_{20}(t) = E_{0\pi} \cos(\omega t + \alpha_2)$$

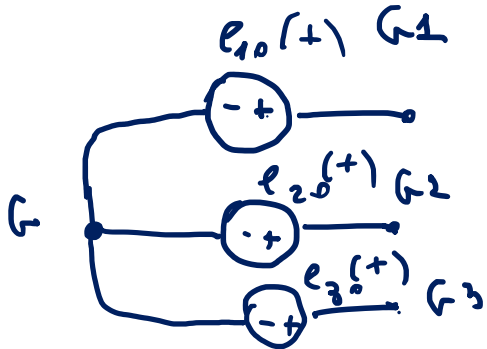
$$e_{30}(t) = E_{0\pi} \cos(\omega t + \alpha_3)$$



$$\alpha_2 = \alpha_1 - \frac{2}{3} \pi$$


$$\alpha_3 = \alpha_2 - \frac{2}{3} \pi$$
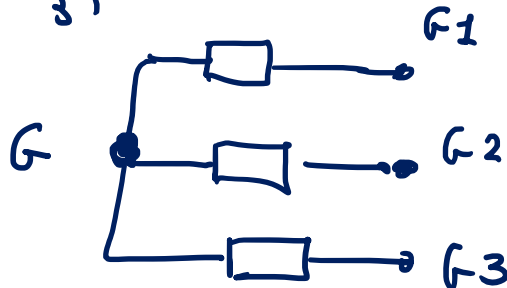
$$\alpha_1 = \alpha_3 - \frac{2}{3} \pi$$



COLLEGAMENTO A STELLA

SISTEMA TRIFASE

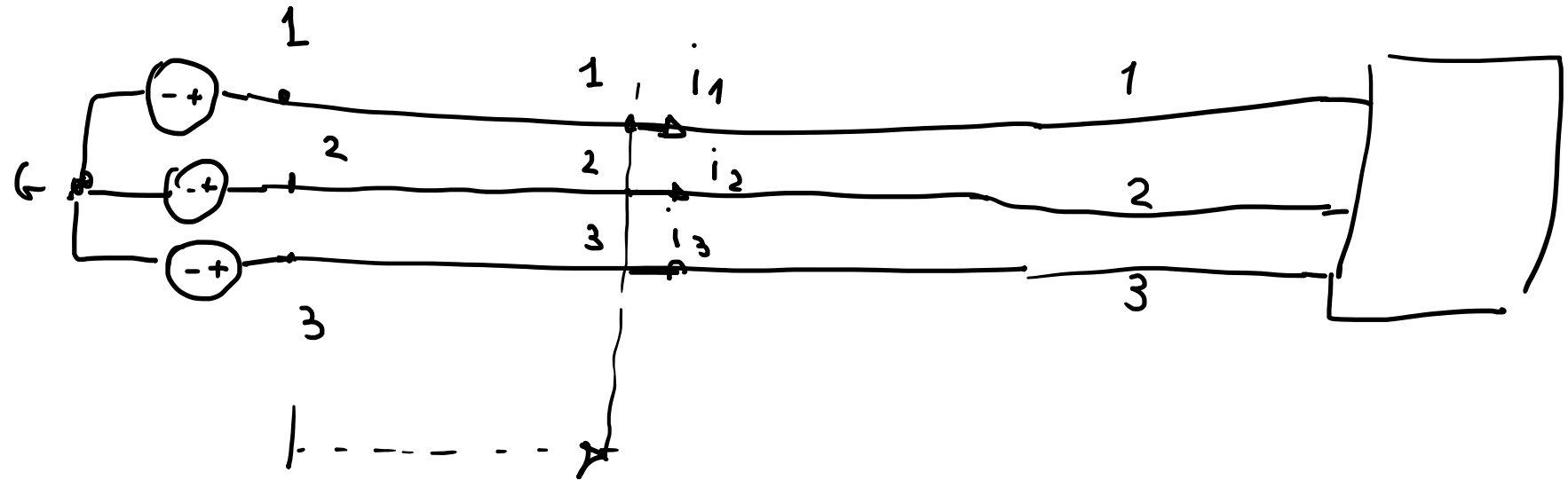

TENSIONI CONCATENATE

$$V_{12}, V_{23}, V_{31}$$

CORRENTI DI LINEA

$$i_1, i_2, i_3$$

SISTEMA SIMMETRICO

$$V_{12,e} = V_{23,e} = V_{31,e}$$

SISTEMA EQUILIBRATO

$$I_{1e} = I_{2e} = I_{3e}$$