

$$\omega = 2\pi f = 2\pi \times 50 = 314.2 \frac{\text{rad}}{\text{s}}$$

$$L = 4 \text{ mH} = 4 \times 10^{-3} \text{ H}$$

$$z_3 = z_{R_2} + z_L = 3 + j 1.257$$

$$z_2 = z_C = -\frac{j}{\omega C} = -\frac{j}{314.2 \times 0.2 \times 10^{-3}} = -j 15.91$$

$$N_{\text{Nodi}} = 2 \quad (N_{\text{Nodi}} - 1) = 1 \text{ LKC.}$$

$$N_{\text{Rami}} = 3 \quad (N_{\text{Rami}} - N_{\text{Nodi}} + 1) = 2 \text{ LKT}$$

$$N_{\text{Rami}} \text{ EQ. COST.}$$

e(t) RIFERIMENTO ANGOLI DI FASE

$$\underline{E} = \frac{E_m}{\sqrt{2}} e^{j0} = \frac{E_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.071$$

$$z_1 = R_1 \quad z_{R_2} = R_2 = 3$$

$$z_1 = 2 \quad z_L = j\omega L = j \times 314.2 \times 4 \times 10^{-3} = j 1.257$$

$$C = 0.2 \text{ mF} = 0.2 \times 10^{-3} \text{ F}$$

$$A) \quad -\underline{I}_{-1} + \underline{I}_{-2} + \underline{I}_{-3} = 0$$

$$\alpha) \quad -\underline{E} + z_1 \underline{I}_{-1} + z_2 \underline{I}_{-2} = 0$$

$$\beta) \quad -z_2 \underline{I}_{-2} + z_3 \underline{I}_{-3} = 0$$

3 EQ.
IN

3 INC.

$\underline{I}_{-1}, \underline{I}_{-2},$
 \underline{I}_{-3}

$$\underline{I}_{-1} = 1.291 - j 0.1603$$

$$i_1(t) = I_{1\pi} \cos(\omega t + \alpha_1)$$

$$\omega = 2\pi f = 314.2 \frac{\text{rad}}{\text{s}}$$


$$I_{1e} = |\underline{I}_{-1}| = \frac{I_{1\pi}}{\sqrt{2}}$$

$$I_{1\pi} = \sqrt{2} \quad I_{1e} = \sqrt{2} \times 1.301 = 1.84 \text{ A}$$

$$I_{1e} = |\underline{I}_{-1}| = \sqrt{1.291^2 + 0.1603^2} = 1.301 \text{ A}$$


$$\underline{I}_{-1} = I_{1e} e^{j\alpha_1} = \underbrace{I_{1e} \cos \alpha_1}_{1.291} + j \underbrace{I_{1e} \sin \alpha_1}_{-0.1603}$$
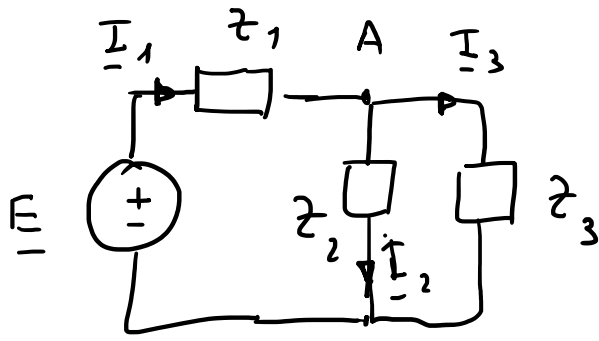
$$\left\{ \begin{array}{l} \cos \alpha_1 = \frac{1.291}{1.301} = 0.9923 \\ \sin \alpha_1 = -\frac{0.1603}{1.301} = -0.1232 \end{array} \right. \Rightarrow \alpha_1 = \sin^{-1}(-0.1232) = -0.1235 \text{ rad} = -7.076^\circ$$




$$z_{23} = \frac{z_2 z_3}{z_2 + z_3} = \frac{-j15.91 \times (3 + j1.257)}{-j15.91 + 3 + j1.257} = 3.395 + j0.6699$$

B

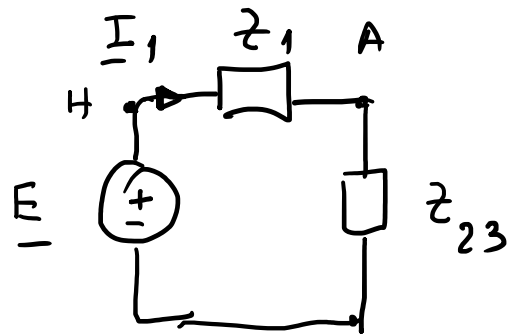
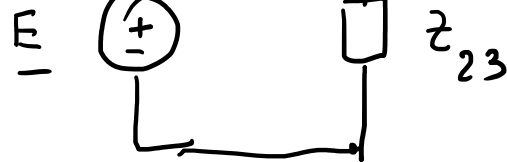
$$I_2 = \frac{V_{AB}}{z_2} = \frac{4.49 + j0.3206}{-j15.91} = -0.02 + j0.2822$$




$$I_3 = \frac{V_{AB}}{z_3} = \frac{4.49 + j0.3206}{3 + j1.257} = 1.311 - j0.4425$$

B


$$V_{AB} = z_{23} I_1 = (3.395 + j0.6699) \times (1.291 - j0.1603) = 4.49 + j0.3206$$

H

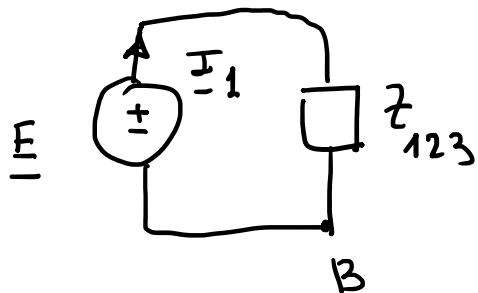

$$I_1 = \frac{E}{z_{123}} = \frac{7.071}{5.395 + j0.6699} = 1.291 - j0.1603$$
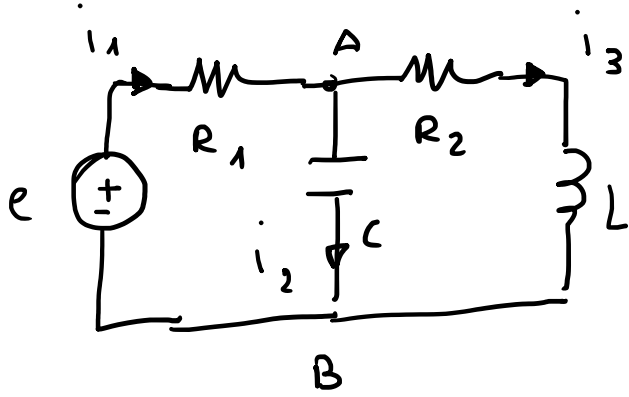
$$z_{123} = z_1 + z_{23} = 2 + 3.395 + j0.6699 = 5.395 + j0.6699$$



$$N_E = \underline{E} \underline{I}_1^* = P_E + jQ_E$$

$$N_E = 7.071 \times (1.291 + j0.1603) = 9.129 + j1.133$$

$$P_E = 9.129 \text{ W}, \quad Q_E = 1.133 \text{ VAR}$$

$$P_{R_1} = R_1 \bar{I}_{1e}^2 = 2 \times 1.301^2 = 3.385 \text{ W}$$

$$I_{1e} = |\underline{I}_1| = \sqrt{1.291^2 + 0.1603^2} = 1.301 \text{ A}$$

$$P_{R_2} = R_2 \bar{I}_{2e}^2 = 3 \times 1.384^2 = 5.746 \text{ W}$$

$$I_{2e} = |\underline{I}_2| = \sqrt{0.02^2 + 0.2822^2} = 0.2829 \text{ A}$$

$$P_{R_1} + P_{R_2} = P_E \quad P_{R_1} + P_{R_2} = 9.131 \text{ W}$$


$$Q_L = \omega L \bar{I}_{3e}^2 = 1.257 \times 1.384^2 = 2.408 \text{ VAR}$$

$$I_{3e} = |\underline{I}_3| = \sqrt{1.311^2 + 0.4425^2} = 1.384 \text{ A}$$

$$Q_C = -\frac{1}{\omega C} \bar{I}_{2e}^2 = -15.91 \times 0.2829^2 = -1.273 \text{ VAR}$$

$$Q_L + Q_C = 1.135 \text{ VAR}$$

$$Q_L + Q_C = Q_E$$

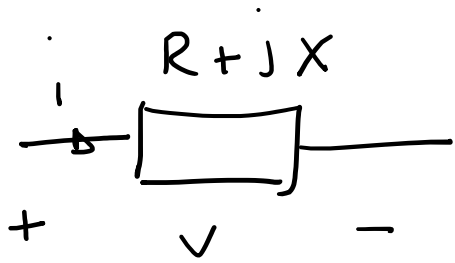


$$N_{ASS} = \underline{V} \underline{I}^* = R I_e^2 + jX I_e^2$$

$$P_{ASS} = R I_e^2 \quad Q_{ASS} = X I_e^2$$

$$N_{EROGATA} = -N_{ASS} = -R I_e^2 - jX I_e^2$$
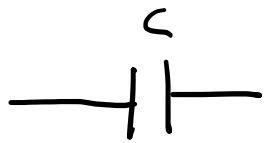
$$P_{EROGATA} = -R I_e^2 \quad Q_{EROGATA} = -X I_e^2$$



$$X = -\frac{1}{\omega C}$$

$$Q_{ASS} = -\frac{1}{\omega C} I_e^2 < 0$$



$$Q_{EROGATA} = \frac{1}{\omega C} I_e^2 > 0$$

RIFASAMENTO

$$e(t) = E_{\text{eff}} \cos(\omega t)$$

$$f = 50 \text{ Hz}$$


$$E_e = 230 \text{ V}$$

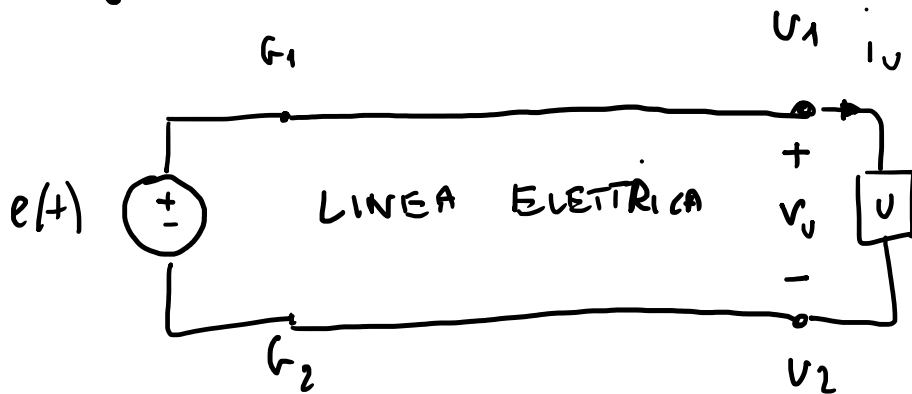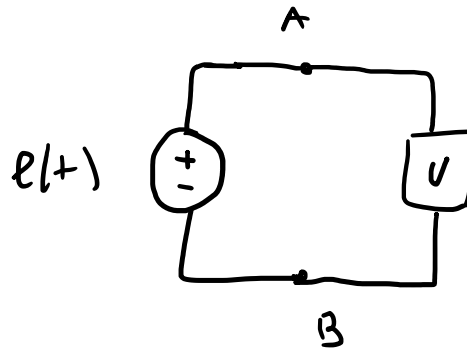

$$P_V = V_{v,e} I_{v,e} \cos(\varphi_V)$$


$$I_{v,e} = \frac{P_V}{V_{v,e} \cos(\varphi_V)}$$
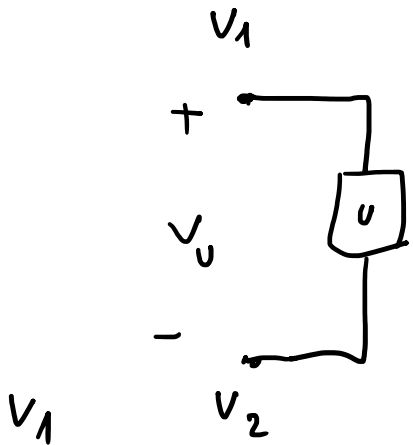
$$Q_V = V_{v,e} I_{v,e} \sin(\varphi_V)$$





$V_{u,e}, P_u, \cos \varphi_u$

$\varphi_u > 0$

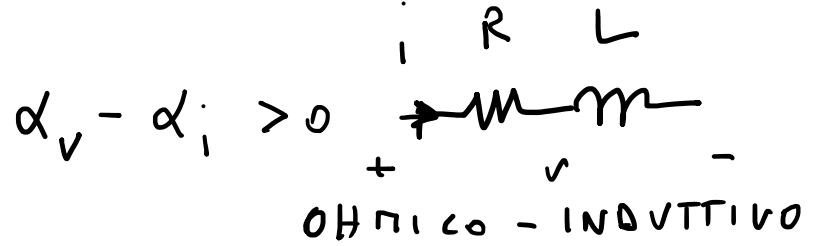

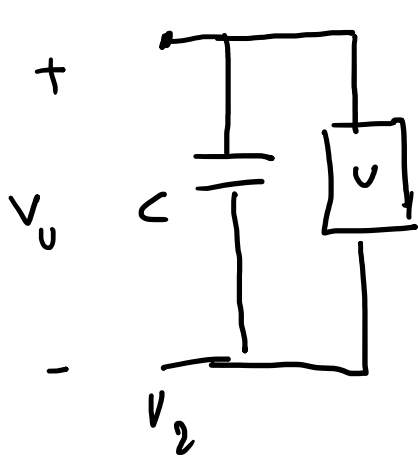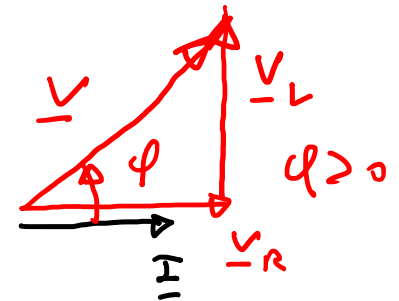
$\underline{V} = \underline{V}_R + \underline{V}_L$




$C = \text{CAPACITÀ DI RIFASAMENTO}$

$P'_u = \cancel{P_c} + P_u$

$Q'_u = Q_c + Q_u$

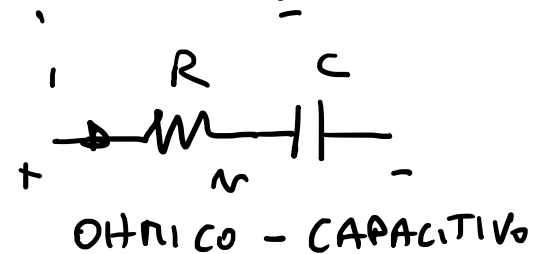

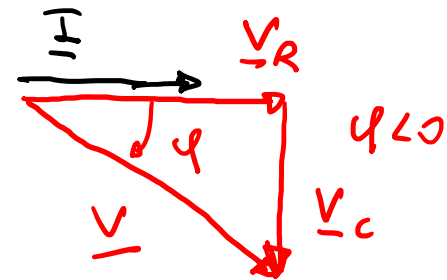
$\underline{V} = \underline{V}_R + \underline{V}_C$



$P = V_e I_c \cos \varphi$

$Q = V_e I_c \sin \varphi$

$\tan \varphi = \frac{Q}{P}$

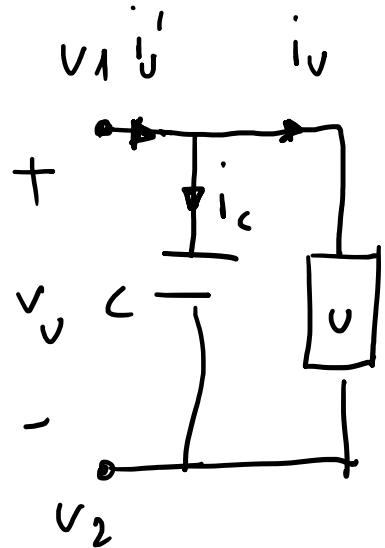

$$P_V' = P_V \quad Q_V = P_V \cdot \tan \phi_V$$


$$Q_V' = Q_C + Q_V \quad Q_V' = P_V' \tan \phi_V'$$

$$\underline{I}_C = \frac{\underline{V}_c}{-\frac{j}{\omega C}} = j\omega C \underline{V}_c \quad I_{ce} = |\underline{I}_C| = \omega C V_{v,e}$$

$$\underline{I}_V' = \underline{I}_V + \underline{I}_C$$

$$Q_C = -\frac{1}{\omega C} I_{ce}^2 = -\frac{1}{\omega C} \omega^2 C^2 V_{v,e}^2 = -\omega C V_{v,e}^2$$
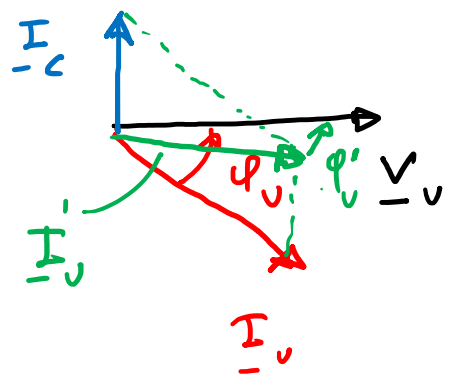
$$P_V' \tan \phi_V' = -\omega C V_{v,e}^2 + P_V \tan \phi_V$$



$$C = \frac{P_V (\tan \phi_V - \tan \phi_V')}{\omega V_{v,e}^2}$$

$$\cos \phi_V' = 0.95$$

$$\phi_V' = \cos^{-1}(0.95)$$

$$I_{v,e}^2 = \frac{P_V}{V_{v,e} \cos(\phi_V')}$$