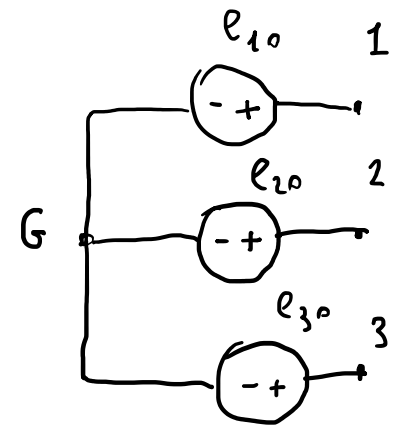


$V_{12}, V_{23}, V_{31}$  TEN. CONCATENATE  
 $i_1, i_2, i_3$  COR. LINEA

LKT 1231  $N_{12}(+) + N_{23}(+) + N_{31}(+) = 0$   $V_{-12} + V_{-23} + V_{-31} = 0$

LkC S  $i_1(+) + i_2(+) + i_3(+) = 0$   $I_{-1} + I_{-2} + I_{-3} = 0$



$e_{10}, e_{20}, e_{30}$  TENSIONI PRINCIPALI DI FASE (STELLATE)

$$\left. \begin{aligned}
 V_{-12} &= E_{-10} - E_{-20} \\
 V_{-23} &= E_{-20} - E_{-30} \\
 \cancel{V_{-31} = E_{-30} - E_{-10}}
 \end{aligned} \right\} +$$

$E_{-10} + E_{-20} + E_{-30} = 0$



$V_{-12} + V_{-23} = E_{-10} - E_{-30} \Rightarrow -V_{-31} = E_{-10} - E_{-30} \quad V_{-31} = E_{-30} - E_{-10}$

$V_{-31} = -V_{-12} - V_{-23}$

SISTEMA TRIFASE SIMMETRICO  $V_{12,e} = V_{23,e} = V_{31,e} = V_e$

$V_{-12} + V_{-23} + V_{-31} = 0$   
DIRETTO  
 1

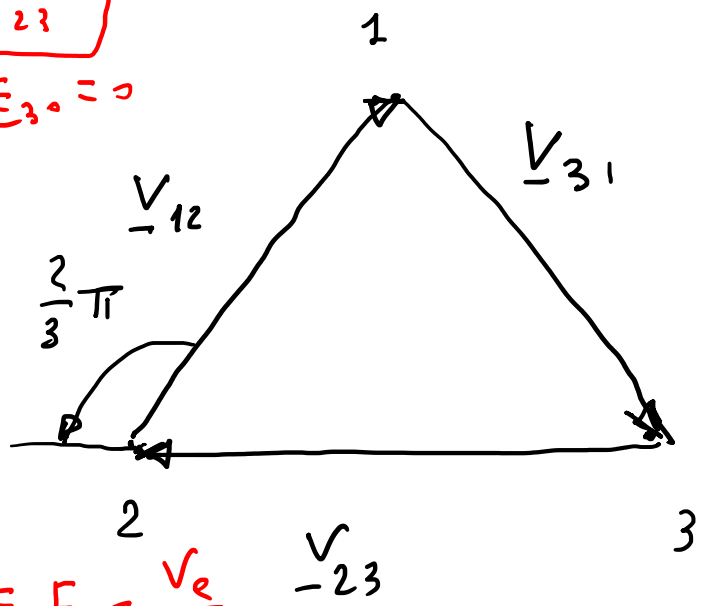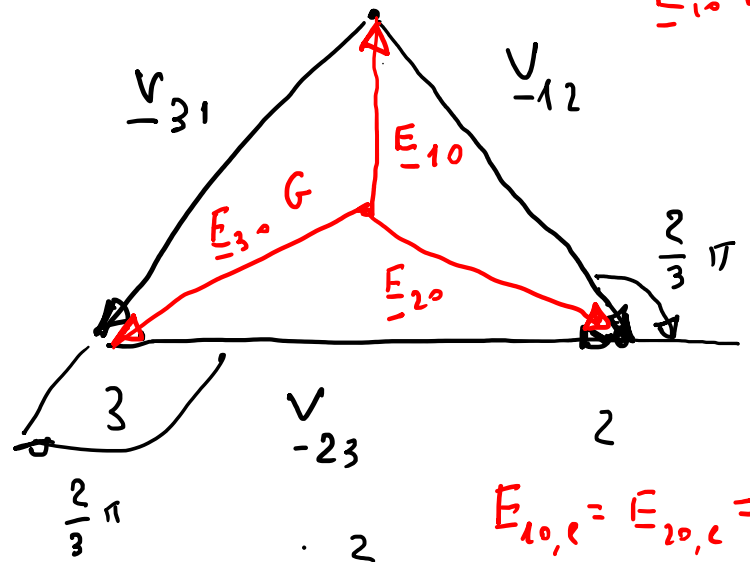
$E_{10} - E_{20} = V_{-12}$     $E_{30} - E_{10} = V_{-31}$   
 $E_{20} - E_{30} = V_{-23}$   
 INVERSO  
 $E_{10} + E_{20} + E_{30} = 0$



$E_{10,e} = E_{20,e} = E_{30,e} = E_p = \frac{V_e}{\sqrt{3}}$

$V_{-23} = V_{-12} e^{-j \frac{2}{3} \pi}$   
 $V_{-31} = V_{-23} e^{-j \frac{2}{3} \pi}$   
 $V_{-12} = V_{-31} e^{-j \frac{2}{3} \pi}$

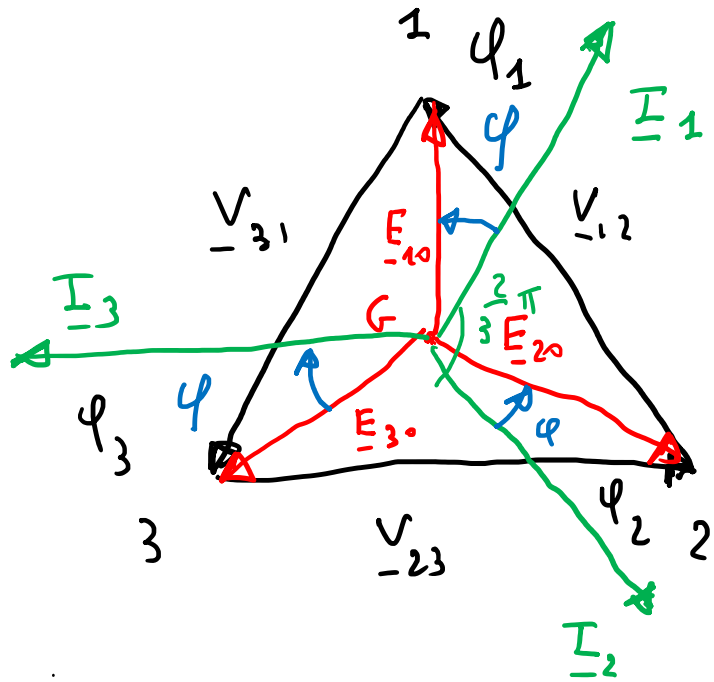$V_{-23} = V_{-12} e^{j \frac{2}{3} \pi}$   
 $V_{-31} = V_{-23} e^{j \frac{2}{3} \pi}$   
 $V_{-12} = V_{-31} e^{j \frac{2}{3} \pi}$



SISTEMA EQUILIBRATO

$$\underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 0$$

$$I_{1,e} = I_{2,e} = I_{3,e} = I_e$$

$$\underline{I}_2 = \underline{I}_1 e^{-j \frac{2}{3} \pi}$$

$$\underline{I}_3 = \underline{I}_2 e^{-j \frac{2}{3} \pi}$$

$$V_{-23} = V_e$$

$$V_{-12} = V_{-23} e^{j \frac{2}{3} \pi} = V_e e^{j \frac{2}{3} \pi}$$

$$V_{-31} = V_{-23} e^{-j \frac{2}{3} \pi} = V_e e^{-j \frac{2}{3} \pi}$$


$$\underline{E}_{10} = \frac{V_e}{\sqrt{3}} e^{j \frac{\pi}{2}}$$

$$\underline{E}_{20} = \underline{E}_{10} e^{-j \frac{2}{3} \pi} = \frac{V_e}{\sqrt{3}} e^{j \left( \frac{\pi}{2} - \frac{2}{3} \pi \right)}$$

$$\underline{E}_{30} = \underline{E}_{10} e^{j \frac{2}{3} \pi} = \frac{V_e}{\sqrt{3}} e^{j \left( \frac{\pi}{2} + \frac{2}{3} \pi \right)}$$

SISTEMA EQUILIBRATO

$$I_{1,e} = I_{2,e} = I_{3,e} = I_e$$

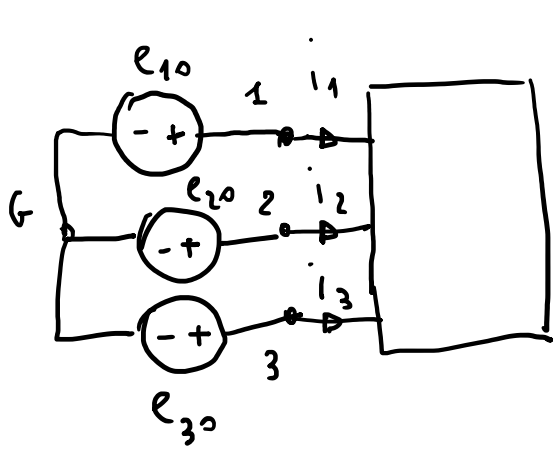

$$P(t) = \sum_{\kappa=1}^3 v_{\kappa 0}(t) i_{\kappa}(t) =$$

$$0 \equiv 2 = v_{12}(t) i_1(t) + v_{32}(t) i_3(t) =$$

$$0 \equiv G = \sum_{\kappa=1}^3 e_{\kappa 0}(t) i_{\kappa}(t)$$

$$P = P_{\text{ATTIVA}} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \sum_{\kappa=1}^3 e_{\kappa 0}(t) i_{\kappa}(t) dt =$$

$$= \sum_{\kappa=1}^3 \frac{1}{T} \int_0^T e_{\kappa 0}(t) i_{\kappa}(t) dt = \sum_{\kappa=1}^3 E_{\kappa 0,e} I_{\kappa,e} \cos(\varphi_{\kappa}) = \sum_{\kappa=1}^3 \frac{V_e}{\sqrt{3}} I_e \cos \varphi$$

$$\varphi_{\kappa} = \alpha_{e_{\kappa 0}} - \alpha_{i_{\kappa}}$$

SIMMETRICO ED EQUILIBRATO

$$E_{\kappa 0,e} = E_e = \frac{V_e}{\sqrt{3}}$$

$$P = 3 \frac{V_e}{\sqrt{3}} I_e \cos \varphi = \sqrt{3} V_e I_e \cos \varphi$$

$$\varphi = \alpha_{e_{\kappa 0}} - \alpha_{i_{\kappa}}$$

$$\varphi_{\kappa} = \varphi$$

$$I_{\kappa,e} = I_e$$

$$N = \sum_{k=1}^3 \underline{E}_{k0} \underline{I}_k^* = P + jQ$$

ΣΥΜΜΕΤΡΙΚΟ ΕΙΔ ΕΞΥΛΙΒΡΑΤΩ

$$\underline{E}_{k0} = \frac{V_e}{\sqrt{3}} e^{j\alpha_{ek0}}$$


$$\alpha_{ek0} - \alpha_{ik} = \varphi$$

$$\underline{I}_k = I_e e^{j\alpha_{ik}}$$

$$N = \sum_{k=1}^3 \frac{V_e}{\sqrt{3}} e^{j\alpha_{ek0}} I_e e^{-j\alpha_{ik}} =$$


$$= \sum_{k=1}^3 \frac{V_e I_e}{\sqrt{3}} e^{j\varphi} = \frac{\sqrt{3} V_e I_e}{\sqrt{3}} e^{j\varphi}$$
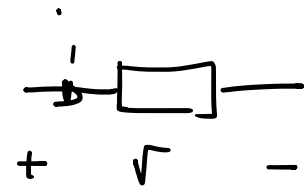
$$= \underbrace{\sqrt{3} V_e I_e \cos \varphi}_{P (W)} + j \underbrace{\sqrt{3} V_e I_e \sin \varphi}_{Q (VAR)}$$



$$P(t) = V(t) i(t)$$

$$N = \underline{V} \underline{I}^*$$

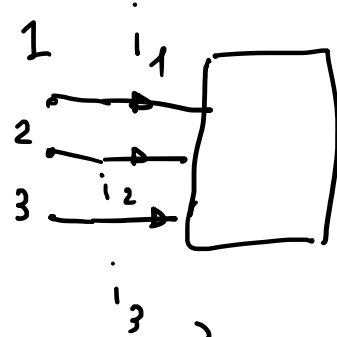

$$P(t) = \sum_{k=1}^3 p_{k0}(t) i_k(t)$$

$$P(t) = N_{12}(t) i_1(t) + N_{32}(t) i_3(t)$$

$$N = \underline{V}_{-12} \underline{I}_1^* + \underline{V}_{-32} \underline{I}_3^*$$

$$A = |N| = |P + jQ| = \sqrt{P^2 + Q^2} = \sqrt{3} V_e I_e$$


(VA)

$$P = \sqrt{3} V_e I_e \cos \varphi = A \cos \varphi$$


$$Q = \sqrt{3} V_e I_e \sin \varphi = A \sin \varphi$$

$$\frac{Q}{P} = \tan \varphi$$
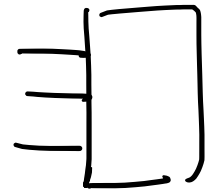
$$I_e = \frac{P}{\sqrt{3} V_e \cos \varphi}$$



$$I_e = \frac{P}{V_e \cos \varphi}$$

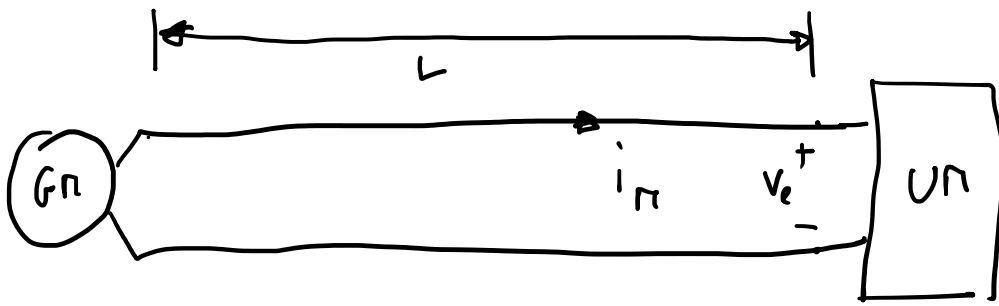


UGUALE COSTO DELLE  
DUE LINEE

UGUALE MATERIALE CONDUTTORE

$$P, \cos \varphi, V_e, P$$

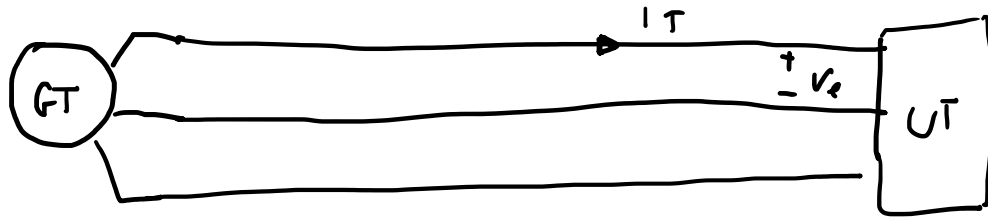VOL = VOLUME DI  
CONDUTTORE  
UTILIZZATO



$$P, \cos \varphi, V_e, P$$

VOL


$$\begin{aligned} \textcircled{P_n} &= 2 \left( P \frac{L}{S_n} \right) \left( \frac{P}{V_e \cos \varphi} \right)^2 \\ &= 2 \cancel{P} \frac{\cancel{L}^2 \times 2}{VOL} \frac{\cancel{P}^2}{\cancel{V_e^2 \cos^2 \varphi}} \end{aligned}$$

$$\frac{P}{P_n} = \frac{3}{4} = 0.75$$

$$VOL = 2 S_n L \quad S_n = \frac{VOL}{2 \times L}$$

$$VOL = 3 S_T L \quad S_T = \frac{VOL}{3 \times L}$$
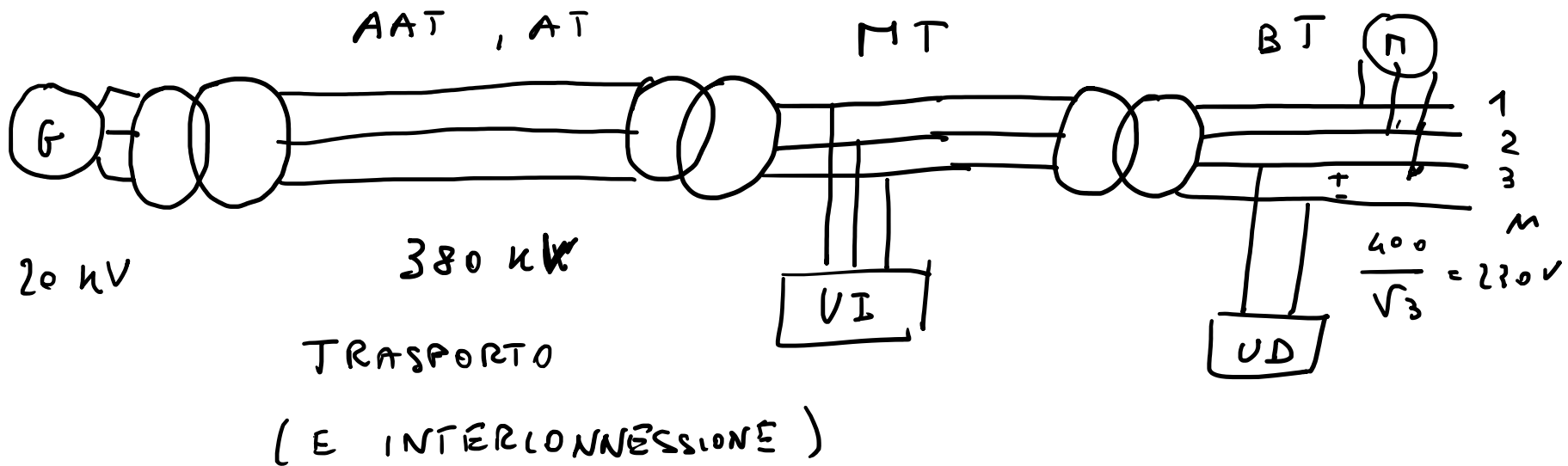
$$\textcircled{P_T} = 3 \left( P \frac{L}{S_T} \right) \left( \frac{P}{\sqrt{3} V_e \cos \varphi} \right)^2 = 3 \cancel{P} \frac{\cancel{L}^2 \times 3}{VOL} \frac{\cancel{P}^2}{\cancel{3} \cancel{V_e^2 \cos^2 \varphi}}$$



$$\bar{I}_e = \frac{P}{\sqrt{3} V_e \cos \varphi}$$

AAT 380 kV  
 AT 130 kV  
 MT = 15 kV

BT  $V_e = 400V$