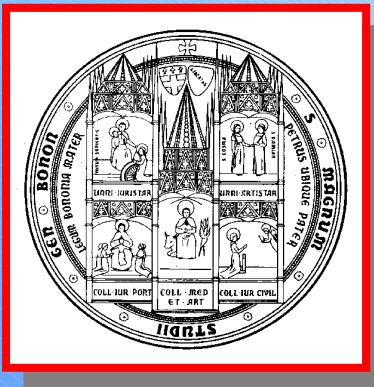


Direct AC/AC Matrix Converters




Dipartimento di Ingegneria Elettrica
Alma Mater Studiorum - Università di Bologna
Viale Risorgimento, 2 - 40136 Bologna

Matrix Converters

- *have received considerable attention in recent years*
 - *may become a good alternative to PWM-VSI topology*
-
- Bi-directional power flow
 - Sinusoidal input/output waveforms
 - Controllable input power factor
 - Compact design, due to the lack of dc-link capacitors for energy storage

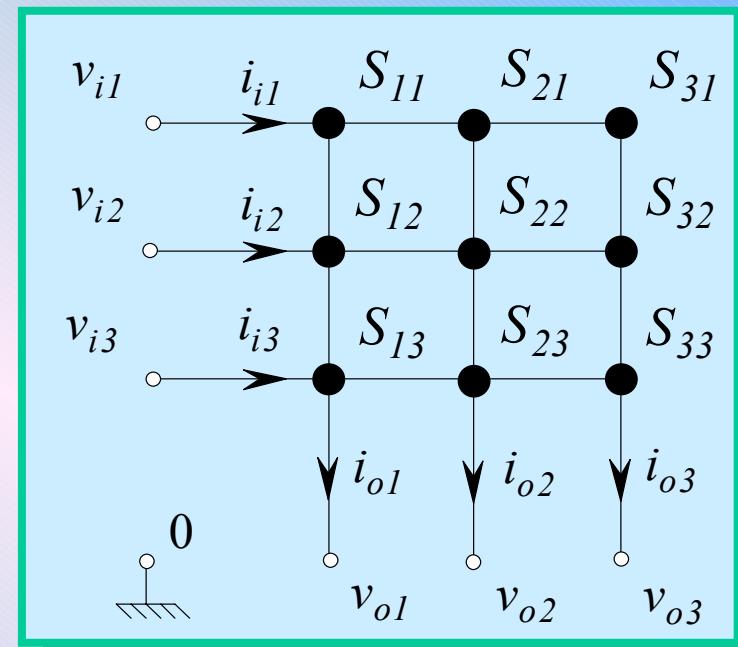Topology complexity of the matrix converter makes study a hard task



*Basic scheme
of matrix converters.*

Space Vector Modulation (SVM) algorithm

SVM completely exploit the possibility of matrix converters to

- control the input power factor regardless the output power factor
- fully utilize the input voltages
- reduce the number of switch commutations in each cycle period.

SVM allows an immediate comprehension of the modulation process


- without the need for a fictitious DC link
- avoiding the addition of the third harmonic components.

Switching Configurations

$$2^9 = 512 \text{ Available}$$



$$27 \text{ Possible}$$

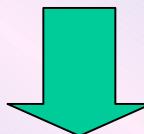

$$21 = 18+3 \text{ usefully employed}$$



Active Configurations

Determine an output voltage vector \bar{v}_o , and an input current vector \bar{i}_i , having fixed directions

Zero Configurations

Determine zero input current and zero output voltage vectors

Switching Configurations Employed

18



3

Switching configuration list	Switches On			v_O	α_O	i_i	β_i
+1	S_{11}	S_{22}	S_{32}	$2/3 v_{12i}$	0	$2/\sqrt{3} i_{o1}$	$-\pi/6$
-1	S_{12}	S_{21}	S_{31}	$-2/3 v_{12i}$	0	$-2/\sqrt{3} i_{o1}$	$-\pi/6$
+2	S_{12}	S_{23}	S_{33}	$2/3 v_{23i}$	0	$2/\sqrt{3} i_{o1}$	$\pi/2$
-2	S_{13}	S_{22}	S_{32}	$-2/3 v_{23i}$	0	$-2/\sqrt{3} i_{o1}$	$\pi/2$
+3	S_{13}	S_{21}	S_{31}	$2/3 v_{31i}$	0	$2/\sqrt{3} i_{o1}$	$7\pi/6$
-3	S_{11}	S_{23}	S_{33}	$-2/3 v_{31i}$	0	$-2/\sqrt{3} i_{o1}$	$7\pi/6$
+4	S_{12}	S_{21}	S_{32}	$2/3 v_{12i}$	$2\pi/3$	$2/\sqrt{3} i_{o2}$	$-\pi/6$
-4	S_{11}	S_{22}	S_{31}	$-2/3 v_{12i}$	$2\pi/3$	$-2/\sqrt{3} i_{o2}$	$-\pi/6$
+5	S_{13}	S_{22}	S_{33}				
-5	S_{12}	S_{23}	S_{32}				
+6	S_{11}	S_{23}	S_{31}	$2/3 v_{31i}$	$2\pi/3$	$2/\sqrt{3} i_{o2}$	$7\pi/6$
-6	S_{13}	S_{21}	S_{33}	$-2/3 v_{31i}$	$2\pi/3$	$-2/\sqrt{3} i_{o2}$	$7\pi/6$
+7	S_{12}	S_{22}	S_{31}	$2/3 v_{12i}$	$4\pi/3$	$2/\sqrt{3} i_{o3}$	$-\pi/6$
-7	S_{11}	S_{21}	S_{32}	$-2/3 v_{12i}$	$4\pi/3$	$-2/\sqrt{3} i_{o3}$	$-\pi/6$
+8	S_{13}	S_{23}	S_{32}	$2/3 v_{23i}$	$4\pi/3$	$2/\sqrt{3} i_{o3}$	$\pi/2$
-8	S_{12}	S_{22}	S_{33}	$-2/3 v_{23i}$	$4\pi/3$	$-2/\sqrt{3} i_{o3}$	$\pi/2$
+9	S_{11}	S_{21}	S_{33}	$2/3 v_{31i}$	$4\pi/3$	$2/\sqrt{3} i_{o3}$	$7\pi/6$
-9	S_{13}	S_{23}	S_{31}	$-2/3 v_{31i}$	$4\pi/3$	$-2/\sqrt{3} i_{o3}$	$7\pi/6$
0 ₁	S_{11}	S_{21}	S_{31}				
0 ₂	S_{12}	S_{22}	S_{32}				
0 ₃	S_{13}	S_{23}	S_{33}				

Active configurations

Zero configurations

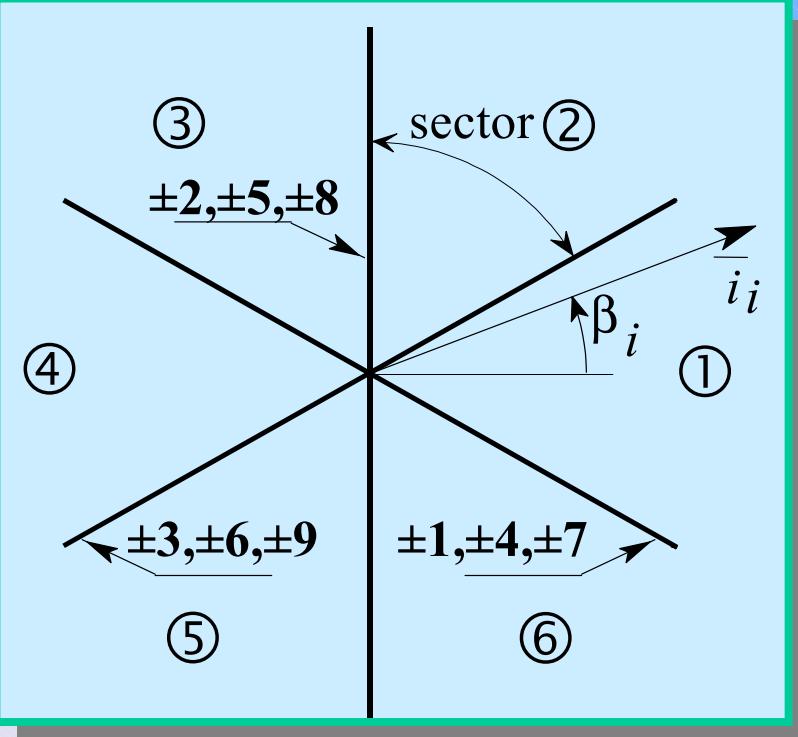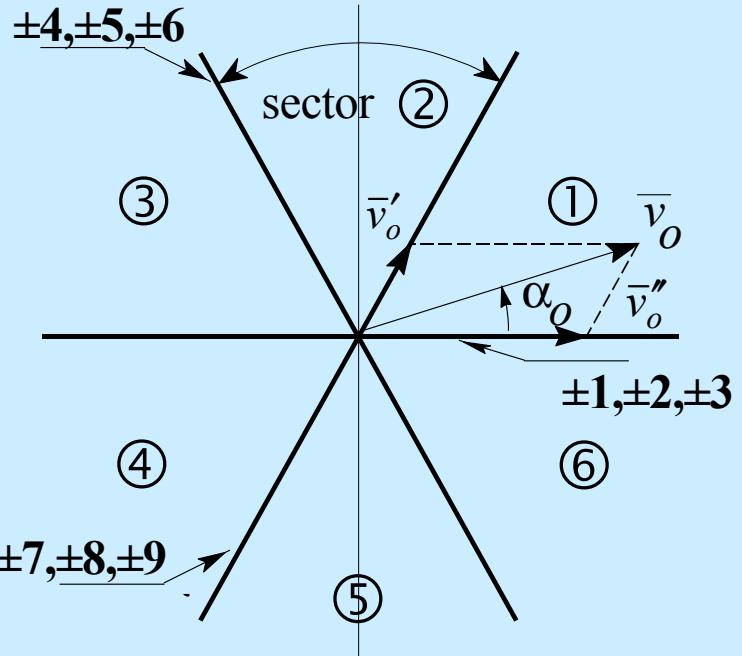Output Voltage and Input Current Space Vectors



*Sectors and directions
of the **output** line-to-neutral
voltage vectors.*


*Sectors and directions
of the **input** current vectors.*

SVM Algorithm

At any sampling instant

\bar{v}_o and φ_i are known (reference quantities)

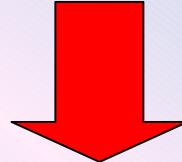\bar{v}_i is imposed by the source (known by measurements)



SVM Algorithm is based on the selection of 4 active configurations that are applied for suitable time intervals within each cycle period T_c .

The zero configurations are applied to complete T_c .

The control of φ_i can be achieved by controlling the phase angle β_i of the input current vector.

SVM algorithm

		Sector of the output voltage vector (K_v)											
		1 or 4				2 or 5				3 or 6			
Sector of the input current vector (K_i)	1 or 4	+9	+7	+3	+1	+6	+4	+9	+7	+3	+1	+6	+4
	2 or 5	+8	+9	+2	+3	+5	+6	+8	+9	+2	+3	+5	+6
	3 or 6	+7	+8	+1	+2	+4	+5	+7	+8	+1	+2	+4	+5
		I	II	III	IV	I	II	III	IV	I	II	III	IV

Selection of the active switching configurations for each combination of

- **output voltage sector**
- **input current sector**

SVM Algorithm

Basic equations of the SVM algorithm

$$\bar{v}_o' = \bar{v}_o^I \delta^I + \bar{v}_o^{II} \delta^{II} = \frac{2}{\sqrt{3}} v_o \cos(\tilde{\alpha}_o - \frac{\pi}{3}) e^{j[(K_v-1)\pi/3 + \pi/3]}$$

$$\bar{v}_o'' = \bar{v}_o^{III} \delta^{III} + \bar{v}_o^{IV} \delta^{IV} = \frac{2}{\sqrt{3}} v_o \cos(\tilde{\alpha}_o + \frac{\pi}{3}) e^{j[(K_v-1)\pi/3]}$$

$$(\bar{i}_i^I \delta^I + \bar{i}_i^{II} \delta^{II}) \cdot j e^{j\tilde{\beta}_i} e^{j(K_i-1)\pi/3} = 0$$

$$(\bar{i}_i^{III} \delta^{III} + \bar{i}_i^{IV} \delta^{IV}) \cdot j e^{j\tilde{\beta}_i} e^{j(K_i-1)\pi/3} = 0$$



To satisfy to the requirements of the

- reference output voltage vector
- input current displacement angle.

Solutions of the Basic Equations

$$\delta^I = (-1)^{K_v+K_i} \frac{2}{\sqrt{3}} q \frac{\cos(\tilde{\alpha}_o - \pi/3) \cos(\tilde{\beta}_i - \pi/3)}{\cos \varphi_i}$$

$$\delta^{II} = (-1)^{K_v+K_i+1} \frac{2}{\sqrt{3}} q \frac{\cos(\tilde{\alpha}_o - \pi/3) \cos(\tilde{\beta}_i + \pi/3)}{\cos \varphi_i}$$

$$\delta^{III} = (-1)^{K_v+K_i+1} \frac{2}{\sqrt{3}} q \frac{\cos(\tilde{\alpha}_o + \pi/3) \cos(\tilde{\beta}_i - \pi/3)}{\cos \varphi_i}$$

$$\delta^{IV} = (-1)^{K_v+K_i} \frac{2}{\sqrt{3}} q \frac{\cos(\tilde{\alpha}_o + \pi/3) \cos(\tilde{\beta}_i + \pi/3)}{\cos \varphi_i}$$

Applied for any combination of
➤ output voltage sector K_v
➤ input current sector K_i

SVM Algorithm

For the feasibility of the control strategy.

$$|\delta^I| + |\delta^{II}| + |\delta^{III}| + |\delta^{IV}| \leq 1$$

Otherwise: the instantaneous values of the input voltages do not allow to satisfy the requirements of output voltage and input power factor.